

Al Mansoura University

Faculty of Engineering

Electronics and Communications Dept.

2nd Year Students

Logic Circuit 2

First Semester 2013

Prepared By: Dr. Muhammad Morsy

Chapter 1: Latches


Lecture No. 1

1.1-Latches.

- ✓ The latch is a type of **temporary storage** device that has **two stable** states (**bistable**) and is normally placed in a category separate from that of flip-flops.
- ✓ Latches are similar to flip-flops because they are **bistable** devices that can **reside** in either of **two states** using a **feedback arrangement**, in which the outputs are connected back to the opposite inputs.
- ✓ The main difference between **latches** and **flip-flops** is in the method used for **changing** their state.

 
1.2- The S-R (SET-RESET) Latch:

- ✓ A latch is a type of **bistable** logic device or **multivibrator**.
- ✓ An **active-HIGH** input S-R (SET- RESET) latch is formed with two cross-coupled **NOR** gates, as shown in Figure 1.1(a).



 (a) Active-HIGH input S-R latch

- ✓ An **active-LOW** input S-R latch is formed with **two cross-coupled NAND** gates, as shown in Figure 1.1 (b).



(b) Active-LOW input \bar{S} - \bar{R} latch

- ✓ Notice that the **output** of each gate is connected to an input of the **opposite gate**.
- ✓ This produces the **regenerative feedback** that is characteristic of all **latches** and **flip-flops**.
- ✓ To **explain** the operation of the latch, we will use the **NAND** gate S-R latch in Figure 1.1 (b).
- ✓ This latch is **redrawn** in Figure 1.2 with the **negative-OR** equivalent symbols used for the **NAND** gates.


 



Figure (1.2)

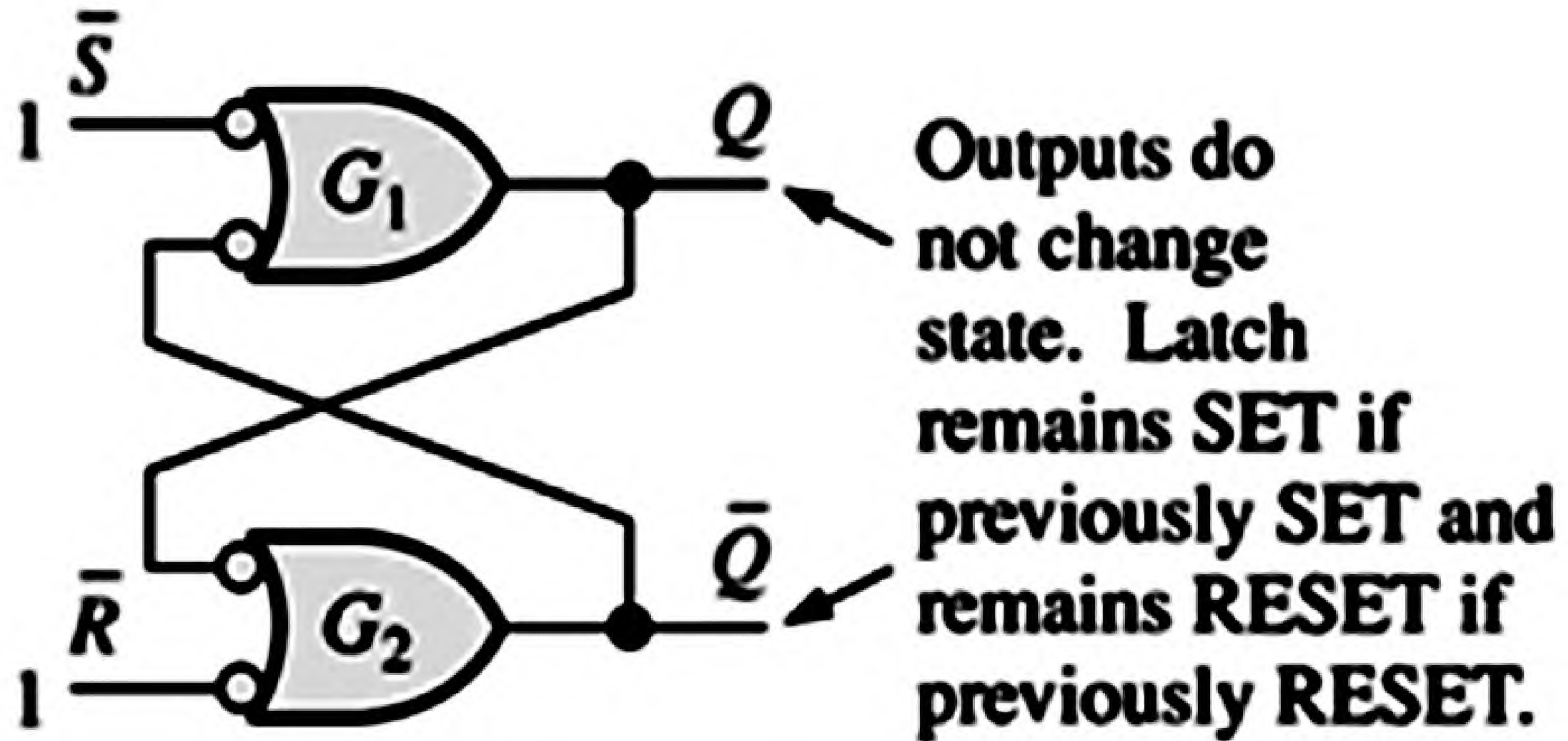- ✓ This is done because **LOWs** on the \bar{S} and \bar{R} lines are the activating inputs.
- ✓ The latch in Figure 1-2 has **two inputs**, \bar{S} and \bar{R} , and **two outputs**, Q and \bar{Q} .
- ✓ Let's start by **assuming that** both inputs and the Q output are **HIGH** as shown in Figure (1.3).




HIGHS on both inputs

- ✓ Since the **Q output** is connected back to an input of gate G_2 , and the \bar{R} input is **HIGH**, the output of G_2 , \bar{Q} must be **LOW**.
- ✓ This **LOW** output is coupled back to an input of gate G_1 ensuring that its output is **HIGH**.
- ✓ When the Q output is **HIGH**, the latch is in the **SET** state.
- ✓ It will remain in this state **indefinitely** until **LOW** is temporarily applied to the \bar{R} input.
- ✓ With a **LOW** on the \bar{R} input and a **HIGH** on \bar{S} , the output of gate G_2 is forced **HIGH**.

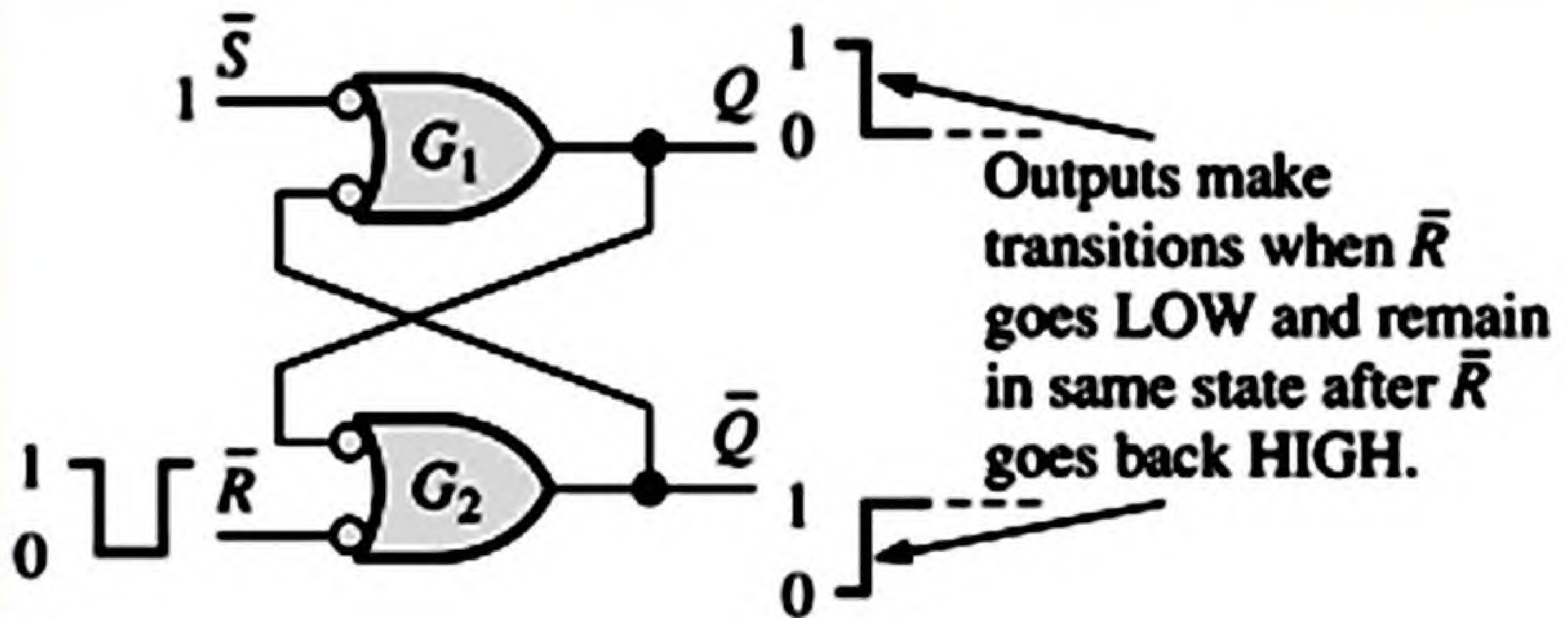

 
- ✓ This **HIGH** on the \overline{Q} output is coupled back to an input of G_1 , and since the S input is **HIGH**, the output of G_1 goes **LOW**.
- ✓ This **LOW** on the Q output is then coupled back to an input of G_2 , ensuring that the \overline{Q} output remains **HIGH** even when the **LOW** on the \overline{R} input is **removed**.




**No transitions occur
because latch is
already RESET.**

Latch starts out RESET ($Q = 0$).

 - ✓ When the **Q output** is **LOW**, the latch is in the **RESET** state.
- ✓ Now the latch remains indefinitely in the **RESET** state until a **LOW** is applied to the S input.
- ✓ In **normal operation**, the **outputs** of a latch are always **complements** of each other.




Latch starts out RESET ($Q = 0$).

 

Latch starts out SET ($Q = 1$).

 - ✓ An **invalid condition** in the operation of an **active-LOW** input S-R latch occurs when **LOWs** are applied to **both** \bar{S} and \bar{R} at the **same time**.




Simultaneous LOWs on both inputs

- ✓ As long as the **LOW** levels are **simultaneously held on** the inputs, both the Q and \bar{Q} outputs are forced **HIGH**, thus **violating** the basic complementary operation of the outputs.
- ✓ Also, if the **LOWs** are released simultaneously, both outputs will attempt to go **LOW**.
- ✓ Since there is always **some small difference** in the **propagation delay time** of the gates, one of the gates will dominate in its transition to the **LOW** output state.


- ✓ This, in turn, **forces** the output of the **slower gate** to remain **HIGH**.
- ✓ In this situation, you cannot **reliably predict** the **next state** of the latch.

Table (1.1) Truth table for an active-LOW input \bar{S} \bar{R} latch.

Inputs		Outputs		Comments
\bar{S}	\bar{R}	Q	\bar{Q}	
1	1	NC	NC	No Change.
0	1	1	0	Latch SET
1	0	0	1	Latch Reset
0	0	1	1	Invalid condition

 


**(a) Active-HIGH input
S-R latch**

 

**(b) Active-LOW input
 \bar{S} - \bar{R} latch**

Figure (1.4) Logic symbols for the S-R and \bar{S} - \bar{R} latch.

 Example (1.1): If the S and R waveforms in the Figure are applied to the inputs of the \bar{S} - \bar{R} latch, determine the waveform that will be observed on the Q output. Assume that Q is initially **LOW**.




State Table

Interval	\bar{S}	\bar{R}	State	Q
0	1	1	Old value, NC	0
1	0	1	Set	1
2	1	1	NC	1
3	1	0	Reset	0
4	1	1	NC	0
5	0	1	Set	1
6	1	1	NC	1


6	1	1	NC	1
7	1	0	Reset	0
8	1	1	NC	0
9	1	0	Reset	0
10	1	1	NC	0
11	0	1	Set	1
12	1	1	NC	1
13	0	1	Set	1
14	1	1	NC	1

 1.3- The Gated S-R Latch.

- ✓ A **gated latch** requires an **enable input**, **EN** (G is also used to designate an enable input). The logic diagram and logic symbol for a gated S-R latch are shown in Figure (1.5).




(a) Logic diagram

 

(b) Logic symbol


- ✓ The S and R **inputs control** the state to which the latch will go when a **HIGH level** is applied to the **EN input**.
- ✓ The latch **will not** change until **EN** is **HIGH**; but as long as it remains **HIGH**, the output is **controlled** by the state of the S and R inputs.
- ✓ In this circuit, the **invalid state** occurs when both S and R are **simultaneously HIGH**.

 Example (1.2): Determine the Q output waveform if the inputs shown in the Figure are applied to a gated S-R latch that is initially **RESET**.



State Table

EN	S	R	State	Q
EN0	X	X	Old	0
EN1	1	0	Set	1
EN2	0	1	Reset	0
EN3	1	0	Set	1
EN4	0	1	Reset	0
EN5	1	0	Set	1

 


- ✓ When S is **HIGH** and R is **LOW**, a **HIGH** on the EN input **sets** the latch.
- ✓ When S is **LOW** and R is **HIGH**, a **HIGH** on the EN input **resets** the latch.

 
1.4- The Gated D Latch.

- ✓ Another type of **gated latch** is called the D **latch**.
- ✓ It **differs** from the S-R latch because it has **only one input** in addition to **EN**. This input is called the **D (data)** input.

- ✓ Figure (1.6) contains a logic diagram and logic symbol of a D latch.



(a) Logic diagram

 


(b) Logic symbol

Figure (1.6) A gated D latch

- ✓ When the **D** input is **HIGH** and the **EN** input is **HIGH**, the latch will **Set**.
- ✓ When the **D** input is **LOW** and **EN** is **HIGH**, the latch will **Reset**.
- ✓ Stated another way, the **output Q follows** the input **D** when **EN** is **HIGH**.

 Example (1.3): Determine the **Q** output waveform if the inputs shown in the Figure are applied to a gated D latch. which is **initially RESET**.





- ✓ When D is **HIGH** and EN is **HIGH**, Q goes **HIGH**.
- ✓ When D is **LOW** and EN is **HIGH**, Q goes **LOW**.
- ✓ When EN is **LOW**, the state of the latch is **not affected** by the D input.

1.5-Edge Triggered Flip-Flop.



- ✓ An **edge-triggered flip-flop** changes state either at the **positive** edge (rising edge) or at the **negative** edge (falling edge) of the clock pulse and is **sensitive** to its inputs only at **this transition** of the clock.
- ✓ **Three** types of edge-triggered flip-flops are covered in this section: S-R, D, and J-K.
- ✓ Although the **S-R flip-flop** is not available in **IC** form, it is the basis for the D and J-K flip-flops.
- ✓ The **logic symbols** for all of these flip-flops are shown in **Figure (1.7)**.

- ✓ Notice that **each type** can be either **positive** edge-triggered (**no bubble** at C input) or **negative edge** triggered (bubble at C input).
- ✓ The key to identifying an edge triggered flip-flop by its logic symbol is the **small triangle** inside the block at the **clock (C) input**.
- ✓ This triangle is called the dynamic input indicator.



Dynamic input
indicator

  

(a) S-R

  

(b) D

  

(c) J-K